

## POWER IN AN AC CIRCUIT

For a dc circuit the power is related to voltage and current as follows:

$$P = V \cdot I$$

In an ac circuit voltage and current depend on time:

$$V \rightarrow v(t) = v_o \cdot \sin(\omega \cdot t)$$

$$I \rightarrow i(t) = i_o \cdot \sin(\omega \cdot t - \Delta\varphi)$$

The instantaneous value of the power at time  $t$  is therefore:

$$p(t) = v(t) \cdot i(t) = v_o \cdot \sin(\omega \cdot t) \cdot i_o \cdot \sin(\omega \cdot t - \Delta\varphi).$$

Using the trigonometric relation


$$\sin \alpha \cdot \sin \beta = \frac{1}{2}(\cos(\alpha - \beta) - \cos(\alpha + \beta)),$$

and the substitutions  $\alpha = \omega \cdot t$  and  $\beta = \omega \cdot t - \Delta\varphi$  we get

$$p(t) = v_o \cdot i_o \cdot \frac{1}{2} \cdot (\cos(\Delta\varphi) - \cos(2 \cdot \omega \cdot t - \Delta\varphi)) = p_o \cdot (\cos \Delta\varphi - \cos(2 \cdot \omega \cdot t - \Delta\varphi))$$

where  $p_o = \frac{1}{2} \cdot v_o \cdot i_o$ .

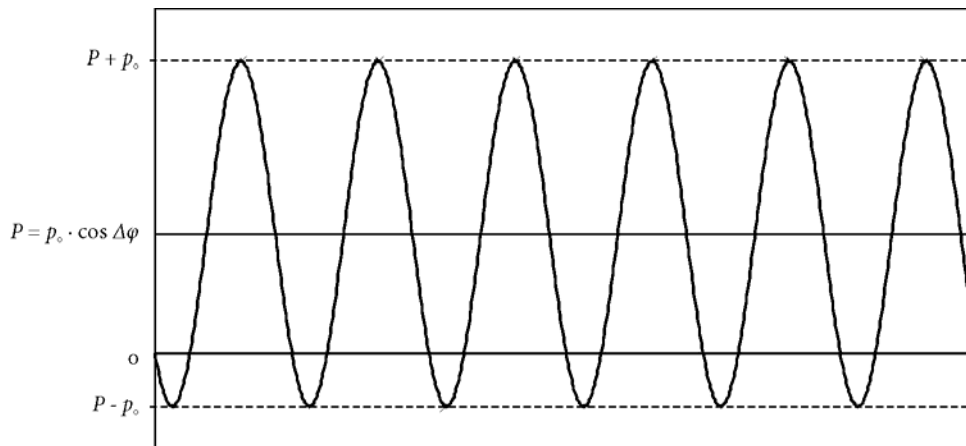We thus find that the power oscillates with amplitude  $p_o$  and twice the frequency of the applied voltage around the average value  $P = \hat{p} \cdot \cos \Delta\varphi$  (see figure).



In most practical applications only the average value of the power is of any importance. From the figure it is obvious that the average power is

$$P = \overline{p(t)} = p_o \cdot \cos \Delta\varphi = \frac{1}{2} \cdot v_o \cdot i_o \cdot \cos \Delta\varphi$$

Using the *root mean squares (rms-values)* or *effective values*  $V_{rms} = \frac{v_o}{\sqrt{2}}$  and  $I_{rms} = \frac{i_o}{\sqrt{2}}$  for the voltage and the current we end up with an expression very similar to the one describing the power in a dc circuit:

In an ac circuit with effective voltage  $V_{rms}$  and effective current  $I_{rms}$ , the *effective power* is

$$P = V_{rms} \cdot I_{rms} \cdot \cos \Delta\varphi,$$

where the product  $S = V_{rms} \cdot I_{rms}$  is the *apparent power* and  $\cos \Delta\varphi$  the *power factor*.

In the data sheet of ac appliances we always find the rms values for voltage and current and the effective power or the power factor.