

PRACTICE TEST: DC CIRCUITS

PART A: SHORT QUESTIONS


Remarks:

- No aids (calculator, FoTa, formula sheet) allowed
- Always express numerical results as rounded decimal numbers (except in ratios)
- Derivation required for numerical results

1. On the reverse side of the sheet, suggest a simple circuit that automatically fades out a light bulb after activating a switch. Can you expect an exponentially decaying current for your circuit? Why?
2. Tick the correct statements.


- ☐ In an RC circuit with half life 2.3 ms the capacitor is fully charged after 4.6 ms.
- ☐ The equivalent resistance of two resistors in parallel is always smaller than each resistor's resistance.
- ☐ When discharging a capacitor, the electric power decreases half as fast as the current.
- ☐ In a parallel circuit the voltage is split in the reciprocal ratio of the resistances.

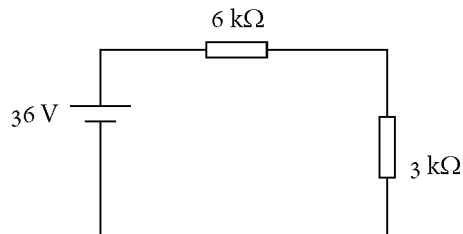3. Calculate the electric power dissipated in the $3\text{ k}\Omega$ resistor.



4. A current divider connected to 12 V splits the current in the ratio 2 : 1. The total current is 6 mA. Calculate the two resistance values.

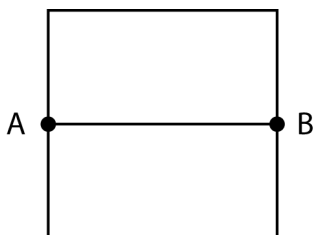5. The figure below is made from a constantan wire. The straight wire connecting points A and B has a resistance of $12\ \Omega$. Calculate the total resistance between A and B.




NUMERICAL SOLUTIONS: 2. ☐ ☒ ☐ ☐; 3. 48 mW; 4. 3 kΩ, 6 kΩ; 5. 6 Ω

PART B: PROBLEMS

Remarks:

- Write your solutions to the problems on the answer sheet. Start a new page for every problem.
- An algebraic solution and all values used in calculations are required to get the full mark.
- Results must be rounded to at most three significant figures.

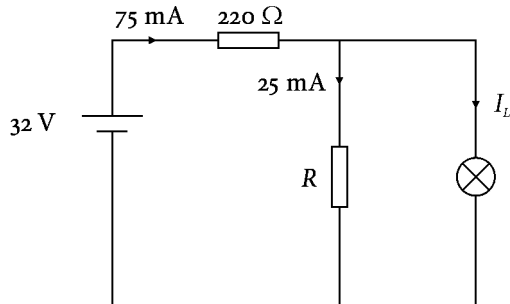
- Two resistors and a light bulb are connected to a battery as described by the circuit diagram below.



- Calculate the total power dissipated in the circuit.
- Determine the current I_L flowing through the light bulb and the resistance R .
Calculate the light bulb's resistance and the power dissipated in it.
- The applied voltage is increased. How does this affect the current through the resistor R ? Give a qualitative explanation for your answer.

- A capacitor is charged through a $2.2 \text{ k}\Omega$ resistor on a voltage of 5.0 V .

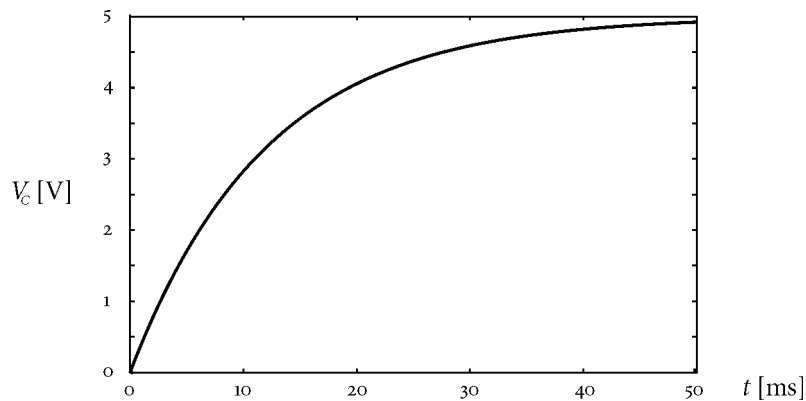The charging process is investigated with an oscilloscope. The result is displayed in the following voltage vs. time graph.



- Determine the half life from the diagram.
Check whether it is sensible to assume an exponential voltage.
- Calculate the circuit's capacitance from the measured half life.
- Draw the current vs. time diagram for this circuit. Label the axes with the correct values.

NUMERICAL SOLUTIONS: 1. 2.4 W , 50 mA , 620Ω , 310Ω , 0.78 W , current increases; 2. 8 ms , $5.2 \mu\text{F}$