

PART A: SHORT QUESTIONS

- No aids (calculator, FoTa, formula sheet) allowed
- Always express numerical results as rounded decimal numbers (except in ratios)
- Derivation required for numerical results

-


- NUMERICAL SOLUTIONS: 2. ☒☐☒☐; 3. $L_4, L_3, L_1 = L_2$; 4. 1.1 V, 5 mA, 5.5 mW; 5. 8 : 1

PART B: PROBLEMS

REMARKS:

- Write your solutions to the problems on the answer sheet. Start a new page for every problem.
- An algebraic solution and all values used in calculations are required to get the full mark.
- Results must be rounded to at most three significant figures.

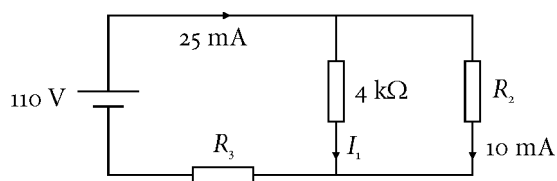1. The heating of an old toaster consists of two identical iron wires. They each have a length of 15 m and a resistance of $48\ \Omega$ (at room temperature). At level 1 (only one wire connected to the voltage supply), the heating power on 230 V is measured to be 210 W.
 - a) Calculate the heating wires' diameter.
 - b) Calculate the heating wires' resistance and temperature while in operation.
 - c) The toaster offers a "booster" level, which has a higher heating power. How are the wires connected in this case and what is the corresponding power?
2. Three resistors are connected to a dc voltage supply as described by the circuit diagram below.



- a) Calculate the total power dissipated by the circuit. What happens to the electric energy?
- b) Determine the missing quantities (I_1 , R_2 , R_3). No formal solutions are required.
- c) The branch of the circuit with the $4\text{ k}\Omega$ resistor is interrupted. How does this affect the potential difference across R_3 and the current through R_2 ? Give qualitative (!) explanations for your answers.

NUMERICAL SOLUTIONS: 1. 0.2 mm, $250\ \Omega$, $705\ ^\circ\text{C}$, 420 W; 2. 2.75 W, 15 mA, $6\text{ k}\Omega$, $2\text{ k}\Omega$, $\Delta V_3 \downarrow$, $I_2 \uparrow$