

INFINITE RESISTOR CHAINS

Find the equivalent resistance between A and B for the following infinite resistor chains.

