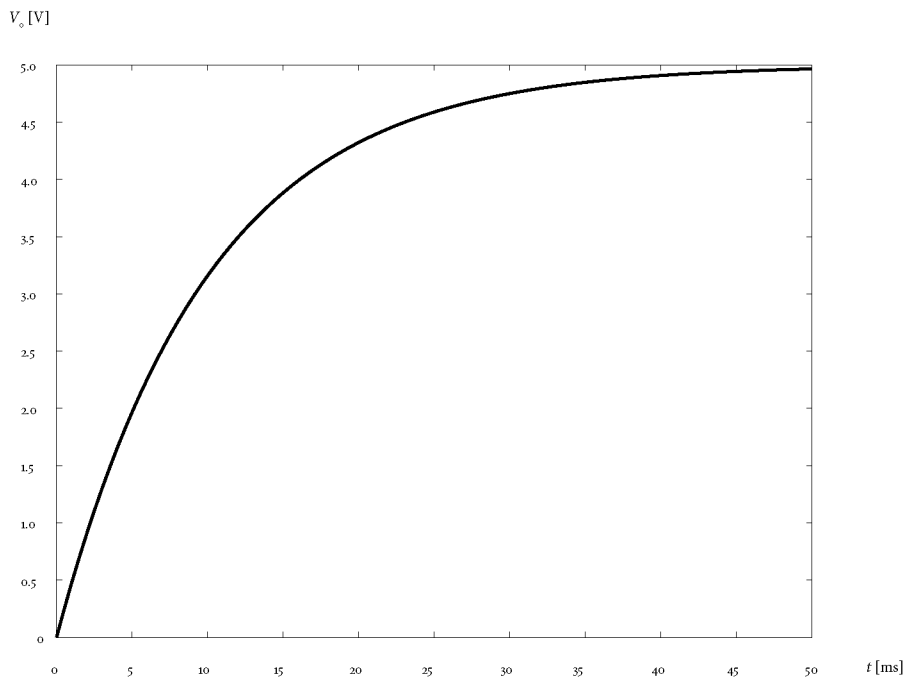


RC CIRCUITS

BASIC PROBLEMS

1. A capacitor with capacitance $100\text{ }\mu\text{F}$ is discharged through a resistor with resistance $330\text{ k}\Omega$. How long does it take until the voltage across the capacitor has decreased to one fourth of its initial value?
2. An empty capacitor and a resistor with resistance $15\text{ k}\Omega$ are connected in series to a 50 V voltage supply. The half life for the charging process is measured to be 0.4 s . Calculate the current flowing 0.2 s after the charging process has started.
3. A capacitor is charged on a voltage of 100 V through a resistor. After 4 s the voltage across the capacitor is 75 V . How long does it take to charge the capacitor to the same voltage if it is connected to 150 V ?
4. The half lives for discharging two different capacitors through the same resistor are 2 s and 4 s , respectively. Calculate the half life when the two capacitors are connected in series or in parallel.
5. A capacitor is charged to 5 V through a resistor with resistance $100\text{ }\Omega$. The charging process is recorded with an oscilloscope. The result of this measurement is displayed in the graph below.
 - a) Determine the half life of the charging process and calculate the time constant and the capacitance.
 - b) Derive a formal expression for the slope of the graph at the time $t = 0$. Read the slope from the diagram and use this expression to calculate the capacitance. Compare the results of a) and b).



ADDITIONAL PROBLEMS

6. A capacitor with capacitance C is discharged through a resistor with resistance R . In analogy to the half life derive a formal expression for the „tenth life“.
7. The energy stored in the capacitor of an RC circuit drops to $23\text{ }\%$ in $1.3\text{ }\mu\text{s}$. How long does it take the voltage across the capacitor to drop to $31\text{ }\%$ of the initial value?
8. A simple flashing light consists of a capacitor with capacitance $2\text{ }\mu\text{F}$ which is charged on 100 V through a resistor with resistance $1\text{ M}\Omega$. A neon bulb is connected in parallel to the capacitor. When the voltage across the capacitor reaches the neon bulb's ignition voltage $V_I = 80\text{ V}$, the bulb lights up and the capacitor is quickly discharged until the bulb goes out at the extinguish voltage $V_E = 70\text{ V}$.
 - a) Sketch the voltage across the capacitor vs. time for several periods.
 - b) How long does it take until the neon bulb lights up for the first time? Calculate the flashing frequency.

SOLUTIONS: 1. 46 s ; 2. 2.4 mA ; 3. 2 s ; 4. 1.3 s and 6 s ; 5. 98 nF , $9.8\text{ }\mu\text{s}$; $0.5\text{ V}/\mu\text{s}$; 6. $RC \cdot \ln 10$; 7. $2.1\text{ }\mu\text{s}$; 8. 3.2 s , 1.25 Hz