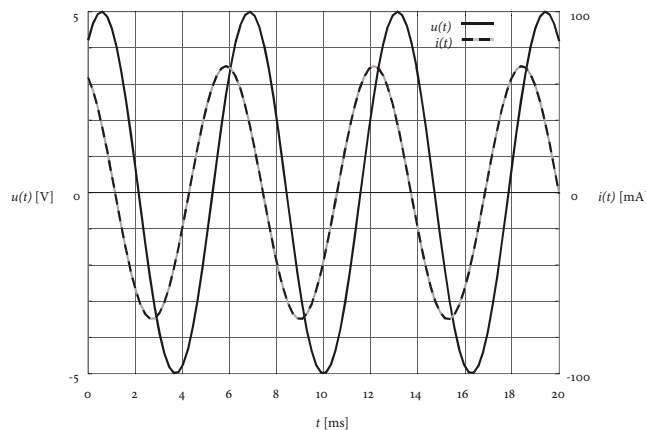


## AC CIRCUITS

- How long does it take for an ac signal with frequency 25 Hz to drop from the maximum to one half?
- A *light emitting diode* (LED) runs on an ac voltage with amplitude 7 V. The current can flow through the diode only in one direction and only when the voltage is greater than the threshold value 2.5 V. Using a construction, determine the fraction of a period during which the LED emits light.
- Using the diagram below, answer the following questions:
  - Determine the amplitude and the period of the voltage signal (solid line). Calculate its rms value, frequency and angular frequency.
  - Determine impedance and phase shift of the circuit and calculate the effective power.



- An ac motor runs on ac voltage with a frequency of 25 Hz and an amplitude of 12 V. Its impedance is  $450 \Omega$ . The current lags behind the voltage by 15 ms. Calculate the current's amplitude and the phase shift.
- The current through a coil on an ac voltage with frequency 2.5 kHz and amplitude 4.8 V is measured to be 18 mA. Calculate the inductance of the coil.
- In the US of America, the household voltage is 110 V/60 Hz. What is the ratio of the current flowing through two identical coils connected to the European and the American household voltage?
- A *capacitor* is an electric part whose impedance is inversely proportional to the frequency:

$$Z_C = \frac{1}{\omega \cdot C},$$

where  $C$  is the *capacitance* of the capacitor. It causes a phase shift of  $90^\circ$  between current and voltage.

Sketch the voltage and current vs. time graphs for a capacitor with capacitance 330 nF on an ac voltage with amplitude 15 V and frequency 50 Hz.

- The impedance of a resistor and a coil in series can be calculated using the following formula:

$$Z = \sqrt{R^2 + Z_L^2}$$

Calculate the current amplitude in a circuit containing a resistor with resistance  $50 \Omega$  and a coil with inductance 15 mH on a voltage with frequency 1.4 kHz and amplitude 24 V.

- An ac motor is labelled as "230 V/0.3 A/50 W". What do these numbers stand for? Calculate the motor's power factor and phase shift.
- A high voltage transformer with 500 turns in its primary and 23'000 turns in its secondary coil is connected to 230 V. Calculate the voltage across the secondary coil.
- The voltage of high voltage power lines shall be increased from 230 kV to 380 kV. By how many percents are the transmission losses reduced?

SOLUTIONS: 1. 6.7 ms; 2.40 %; 3. 5 V, 6.2 ms, 3.5 V, 160 Hz,  $1'000 \text{ s}^{-1}$ ;  $70 \Omega$ ,  $1.0 \text{ rad} = 58^\circ$ ; 4. 27 mA,  $3\pi/4 = 135^\circ$ ; 5. 17 mH; 6. 5 : 2; 8. 170 mA; 9. 0.72,  $43.5^\circ$ ; 10. 10.6 kV; 11. -63 %